

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17MT35

Third Semester B.E. Degree Examination, Dec.2018/Jan.2019 Analog and Digital Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. What is filter? Explain its classification? (04 Marks)
b. Explain the following :
i) 3 dB cut-off frequency
ii) Bandwidth of the filter
iii) Mid band gain of the filter. (06 Marks)
c. Explain the frequency Responses of High Pass Filter (HPF), Band Pass Filter (BPF) and Band Reject Filter (BRF). Mark the midband gain and width in all the responses. (10 Marks)

OR

- 2 a. Design a first order Butterworth HP filter with cut-off frequency of 1KHz and pass band gain of 2. Plot the frequency response. (10 Marks)
b. Design and second order Butterworth LPF at a high cut-off frequency of 2KHz. Plot the frequency response with the mid band gain. (10 Marks)

Module-2

- 3 a. Derive the equations that explain the two criteria required to be fulfilled for oscillator. (10 Marks)
b. With a neat circuit diagram, explain phase shift RC oscillator. (05 Marks)
c. Design the phase shift oscillator for frequency of oscillation $f_0 = 300\text{Hz}$. (05 Marks)

OR

- 4 a. With the help of I/P and O/P waveforms explain the working of zero crossing detector. (10 Marks)
b. For Schmitt trigger circuit, explain the following :
i) Upper Trigger Point (UTP)
ii) Lower Trigger Point (LTP)
iii) Plot of Hysteresis Voltage. (10 Marks)

Module-3

- 5 a. List the five features of 555 Timer. (05 Marks)
b. With a neat circuit diagram, explain the astable operation of 555 Timer. (07 Marks)
c. Explain the architecture of 555 Timer. (08 Marks)

OR

- 6 a. Explain the connection diagram of 555 timer for using it as monostable multi-vibrator. (08 Marks)
b. What is the importance of the following pins in 555 timer, when it is used as monostable multi-vibrator.
i) Trigger Pin (PIN 2) ii) Rest Pin (PIN 4) (08 Marks)
c. Explain the operation of 555 Timer as monostable multi-vibration with waveforms. (04 Marks)

Module-4

- 7 a. Explain the full adder circuit with the following :
 i) Truth table ii) Logic Diagram. (10 Marks)
 b. Explain the working of 4×1 MUX with operation table, select lines and logic diagram. (10 Marks)

OR

- 8 a. Map the following function on K' map $F(A, B, C, D) = \sum 1, 5, 6, 9, 14, 15$. (06 Marks)
 b. Implement the following function using 4×1 MUX. $F(A, B, C) = \sum 1, 3, 5, 7$. (10 Marks)
 c. Draw the K' map for three variables. (04 Marks)

Module-5

- 9 For JK Flip Flop (FF) give the following :
 a. Logic diagram
 b. Graphic symbol
 c. Characteristics table
 d. Characteristic equation. (20 Marks)

OR

- 10 a. Design BCD ripple counter with the following details.
 i) State diagram ii) Logic diagram iii) Timing diagram. (10 Marks)
 b. Design synchronous up counter with the following details :
 i) Count sequence ii) Logic diagram iii) Input equation for each flip-flop. (10 Marks)
