

# CBCS SCHEME

USN

1A1202T1-1

18MT62

Sixth Semester B.E. Degree Examination, July/August 2022

## Power Electronics

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Explain the switching characteristics of Diode. (10 Marks)  
b. Draw the V - I characteristics of MOSFET and briefly explain the same. (06 Marks)  
c. Give the comparison between MOSFET and IGBT. (04 Marks)

OR

- 2 a. With neat diagram explain switching characteristics of IGBT. (10 Marks)  
b. How devices are protected against  $\frac{di}{dt}$  and  $\frac{dv}{dt}$ ? (05 Marks)  
c. Explain the peripheral effects of power electronics equipment. (05 Marks)

### Module-2

- 3 a. Explain the turn-on and turn-off characteristics of SCR with neat diagrams. (10 Marks)  
b. Explain with the help of a circuit diagram and relevant waveforms the commutation of a SCR using an LC circuit. (10 Marks)

OR

- 4 a. Explain with necessary figures the principle of an auxiliary thyristor assisted commutation (class C) circuit. (10 Marks)  
b. An UJT used in a relaxation oscillator circuit is having  $\eta = 0.7$ ,  $V_V = 1V$  and the supply voltage to the circuit is 15V. Design the suitable values of R and C given that the frequency of oscillation is 1KHz. Peak current is 1mA and valley current is 8mA. (10 Marks)

### Module-3

- 5 a. Derive the equations for rms output voltage of a single phase AC controllers with inductive load. (10 Marks)  
b. A single phase half wave controlled rectifier is used to supply power to  $10\Omega$  load from 230V, 50Hz supply at a firing angle of  $30^\circ$  calculate : (10 Marks)  
i) Average output voltage  
ii) Effective output voltage  
iii) Average load current.

OR

- 6 a. Find the power consumed in the heater element shown in Fig.Q6(a) if both SCRs are triggered with delay angle of  $45^\circ$ .

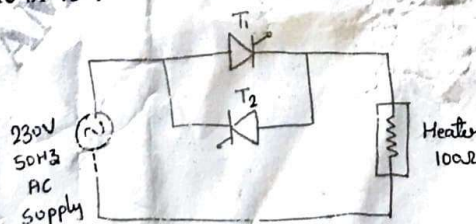


Fig.Q6(a)

(10 Marks)

- b. Explain the operation of a 3 $\phi$  full wave fully controlled bridge rectifier with R load. (10 Marks)

Module-4

- 7 a. Describe the principle of a step down chopper of resistive load. With the help of schematic and wave diagram. Derive an expression for the output voltage. (10 Marks)
- b. A DC chopper has a resistive load of  $20\Omega$  and input voltage  $V_s = 220V$ . when the chopper is on, its voltage drop is  $1.5V$  and chopping frequency is  $10KHz$ . If duty cycle is  $80\%$  determine the average output voltage, rms output voltage and chopper on time. (05 Marks)
- c. Explain briefly how the choppers are classified. (05 Marks)

OR

- 8 a. Explain the operation of impulse cumulated thyristor chopper. (10 Marks)
- b. A step up chopper has input voltage of  $220V$  and output voltage of  $660V$ . If the non conducting time of thyristor chopper is  $100\mu sec$ , compute the pulse width of output voltage. In case pulse width is halved for constant frequency operation, find new output voltage. (10 Marks)

Module-5

- 9 a. Giving neat circuit diagram and waveforms, explain the working of single phase half bridge inverter with RL load. (10 Marks)
- b. With the help of neat diagram and waveforms explain an operation of  $180^\circ$  mode of  $3\phi$  inverters. (10 Marks)

OR

- 10 a. Explain the comparison between  $180^\circ$  conduction mode and  $120^\circ$  conduction mode of  $3\phi$  inverter. (10 Marks)
- b. What is PWM? What are the various PWM techniques? How do they differ from each other? (10 Marks)

\*\*\*\*\*